

333454(28)BE (4th Semester)

Examination, April - May, 2017

[New Scheme]

Analog Electronics Circuits

Time Allowed : 3 hours

Maximum Marks : 80

Minimum Pass Marks : 28

Note : (i) All questions are compulsory. Part (a) of each question is compulsory. Attempt any two parts from (b), (c) and (d) of each question.

(ii) The figures in the right-hand margin indicate marks.

1. (a) Write down the value of n_{fe} , h_{re} , h_{ie} and h_{oe} . [2]
- (b) Explain Miller theorem and Dual of Miller theorem. [7]
- (c) Derive H parameter model for CB and CC configuration. [7]

(d) Prove that $y_o = h_o \left(\frac{R_i + R_{i\infty}}{R_i + R_{i0}} \right)$

where $R_{i\infty} = R_i$ for $R_L = \infty$

and $R_{i0} = R_i$ for $R_L = 0$


[7]

2. (a) Draw the circuit diagram and small signal equivalent circuit for an emitter follower stage at high frequencies. List its three most important characteristics. [2]
- (b) What are hybrid π capacitance? Show that diffusion capacitance is proportional to emitter bias current I_E . [7]
- (c) Derive the expression for transconductance g_m . How transconductance varies with temperature? [7]
- (d) Give the following parameters measurement made at room temperature :
 - $I_C = 5 \text{ mA}$
 - $V_{CE} = 10 \text{ V}$
 - $n_{fe} = 100$
 - $h_{ie} = 60 \Omega$
 - $A_i = 10$ at 10 MHz
 - $C_i = 3 \text{ pF}$
 Find I_B , F_T , C_e , $r_{b'e}$, and $r_{bb'}$ [7]

3. (a) Define Bandwidth of an amplifier. [2]
 (b) Write a short note on Darlington configuration. [7]
 (c) Prove that $F^*_{H} = F_H \sqrt{2^{1/n} - 1}$ in non-cascading stage. [7]
 (d) Define noise. Explain shaft key noise and also explain noise figure. Find the noise bandwidth B_n for an amplifier for which

$$A_{V_0} = 1, F_L = 0\text{Hz and } |A_V(F)| = \frac{1}{\sqrt{1 + (F/F_H)^2}} \quad [7]$$

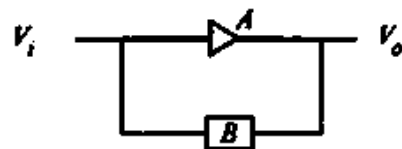4. (a) Define positive and negative feedback. [2]
 (b) Write down the comparison between voltage series, current series, voltage shunt and current shunt. [7]
 (c) Calculate the value of R_{IF} and R_{OF} for current shunt and voltage shunt feedback circuit. [7]
 (d) An amplifier open loop voltage gain $A_v = 1000 + 100$ is available. It is necessary to have an amplifier whose voltage gain varies by no more than ± 1 percent tilt.



- (i) Find the reverse transmission factor β of the feedback n/w used. [7]
 (ii) Find the gain with feedback. [7]
 5. (a) Define Barkhausen criteria. [2]
 (b) Explain frequency stability of oscillator. [7]
 (c) Explain Hartley oscillator. [7]
 (d) Explain Wien Bridge oscillator. [7]