

**328353(28)**

**C. E. (Third Semester) Examination, April-May 2016**

**(New Scheme)**

**(Et & T Engg. Branch)**

**ELECTRONIC DEVICES and CIRCUITS**

*Time Allowed : Three hours*

*Maximum Marks : 80*

*Minimum Pass Marks : 28*

*Note : Attempt all questions. Part (a) of each question is compulsory. Attempt any two parts out of (b), (c) and (d). Answer should be in brief & to the points. Assume suitable data, wherever necessary.*

**Unit-I**

1. (a) Define Mass Action Law. 2
- (b) Find the conductivity of Germanium : 7

**328353(28)**

**PTO**

- (i) Under intrinsic conduction at 300°K.
- (ii) Under acceptor impurity of 1 in  $2 \times 10^7$ .

Given that for Ge,  $n_i$  at 300°K is  $2.5 \times 10^{13} / \text{cm}^3$  and mobility of electrons and holes are 3,800  $\text{cm}^2/\text{V-s}$  and 1,800  $\text{cm}^2/\text{V-s}$  respectively. Number of Ge atoms/ $\text{cm}^3 = 4.4 \times 10^{22}$ .

- (c) Derive the continuity equation for holes in an elementary volume of the semiconductor. Write the corresponding continuity equation for electrons. 7
- (d) Derive expression for contact difference of Potential in an open circuited step graded P-N junction. 7

### Unit-II

- (a) What is the feature of Ideal Diode? 2
- (b) A Ge (Germanium) diode operates at a forward voltage of 0.2 volt. Calculate the factor by which the current will get multiplied when the temperature is increased from 25°C to 75°C. (assumed  $n = 1$ ) 7
- (c) A full wave P-N diode rectifier uses load resistor of 1500  $\Omega$  no filter is used. Assume each diode to have idealized characteristic with  $R_f = 12 \Omega$  and

$R_r = \infty$ . Cut in voltages may be neglected sinewave voltage applied to each diode has amplitude of 32 volts and free of 50 Hz. Calculate : 7

- (i) D. C. Current
- (ii) D. C. Voltage
- (iii) D. C. power o/p
- (iv) A. C. i/p power
- (v) Rectifier efficiency
- (vi) Ripple factor
- (vii) Form factor

- (d) What is the difference between Zener Diode & Normal Diode? Why Zener diode is preferred in voltage regulator ckt? 7

### Unit-III

- 3. (a) Define Transistor biasing. 2
- (b) Describe briefly the basic steps in the construction (fabrication) of Diffused Planar Transistor. 7
- (c) In a Ge PNP transistor, the resistivities of the emitter

and base regions are respectively  $4 \Omega\text{-cm}$  and  $400 \Omega\text{-cm}$ . The average time of electrons in the emitter region is  $\tau_n = 1 \mu\text{s}$ , base width  $w = 20 \text{ Nm}$ . Compute the approximate  $\alpha$  of the transistor, given that  $D_n = 99 \text{ cm}^2/\text{V-s}$ .

(d) Define the stability factor  $S$ ,  $S^I$  (or  $S_V$ ) and  $S^{II}$  (or  $S_\beta$ ) and also specify the condition for avoiding thermal runaway.

#### Unit-IV

4. (a) Draw symbols & polarity conventions for n-channel JFET.
- (b) An n channel FET has  $a = 4 \times 10^{-4} \text{ cm}$  and  $N_D = 0.8 \times 10^{15} \text{ electrons/cm}^3$ . Find Pinch off voltage  $V_p$ . Given that :

$$\epsilon_0 = \frac{1}{36\pi \times 10^9} \text{ F/m} \quad \& \quad \text{relative dielectric}$$

constant of Si is 12.

- (c) Draw & explain self bias configuration of JFET. 7
- (d) Explain the following : 7
- (i) Amplification factor of FET 2
- (ii) FET and voltage variable resistor 5

#### Unit-V

5. (a) Draw symbol of N channel depletion MOSFET & P channel enhancement MOSFET. 2
- (b) With the help of circuit diagram explain potential divider bias for E-MOSFET. 7
- (c) Explain difference between D-MOSFET & E-MOSFET & also explain depletion MOSFET with the help of its structure, drain characteristics & transfer characteristics. 7
- (d) Explain complementary MOSFET with help of its structural diagram. 7