
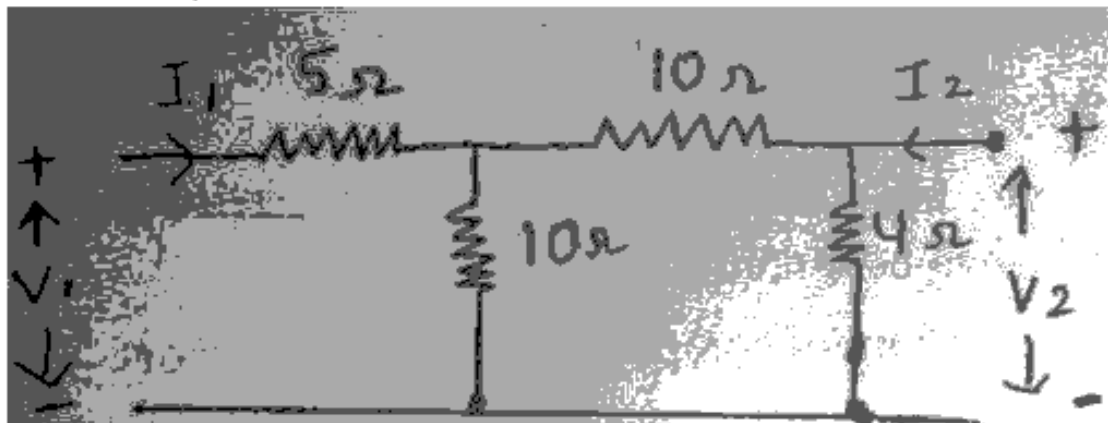


Chapter 1

- | | | |
|---|--|---|
| 1 | Define Thevenin's theorem. | 2 |
| 2 | Find the z-parameter of the network shown. | 7 |

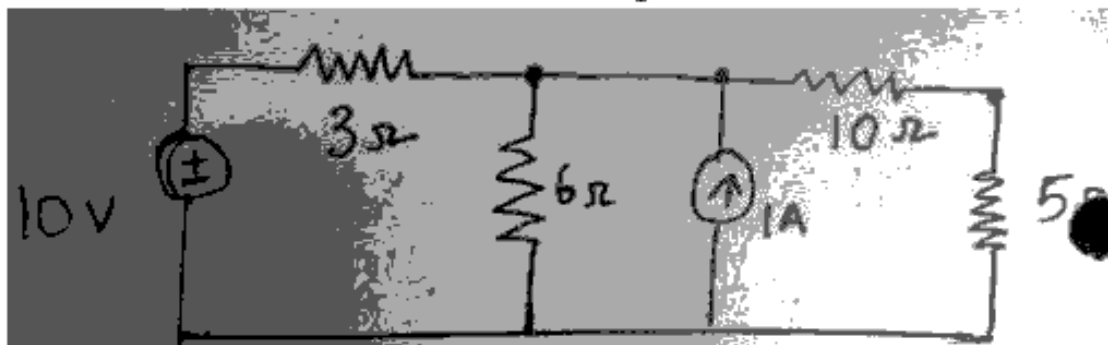

- | | | |
|---|--|---|
| 3 | State and prove maximum power transfer theorem. | 7 |
| 4 | Find the current in 5 Ω Resistor using Norton's theorem. | 7 |



Chapter 2


- | | | |
|---|--|---|
| 1 | What is an Ideal Diode. | 2 |
| 2 | Define transition capacitance of a P-N junction diode and obtain the expression for transition capacitance. | 7 |
| 3 | Explain the working of full wave rectifier and find the expression for its transformer utilization factor (TUF). | 7 |
| 4 | Draw the circuit diagram of capacitor filter and explain its working. | 7 |

Chapter 2

- 1 What is an Ideal Diode. 2
- 2 Define transition capacitance of a P-N junction diode and obtain the expression for transition capacitance. 7
- 3 Explain the working of full wave rectifier and find the expression for its transformer utilization factor (TUF). 7
- 4 Draw the circuit diagram of capacitor filter and explain its working. 7

Chapter 3

- 1 Why base is lightly doped ? **CSVТУonline.com** 2
- 2 Draw and explain output characteristics of common base configuration. 7
- 3 Explain current component in PNP transistor. 7
- 4 A silicon transistor with $V_{BEsat} = 0.8\text{ V}$, $\beta = 100$, $V_{CEsat} = 0.2$ is used in the circuit shown. Find the minimum value of R for which transistor remains in saturation. 7

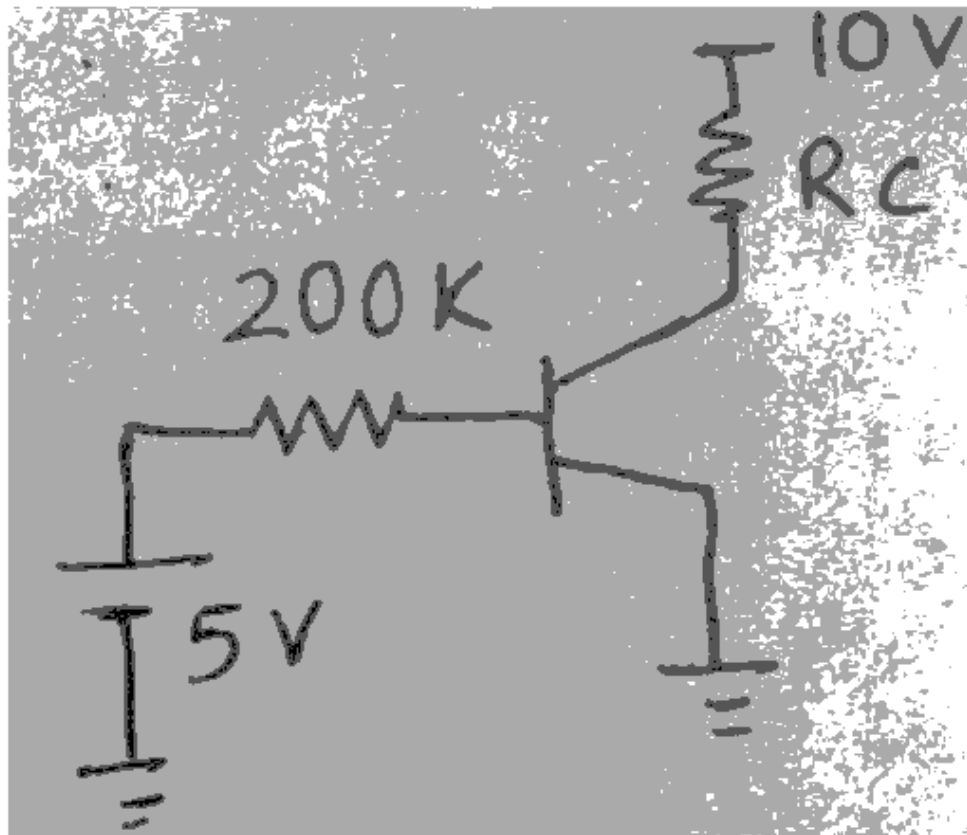


Chapter 4

CSVТУonline.com

- 1 List the three sources of instability of collector current. 2
- 2 Draw the circuit diagram of CE amplifier with diode compensation for I_{CO} . 7

- 3 Draw and explain the working of collector to base bias and find the expression for stability factor S . 7
- 4 For a silicon transistor with $\beta = 50$, $V_{BE} = 0.7$, $V_{CC} = 22.5$ V and $R_C = 5.6$ K is used in the fig shown it is desired to establish Q point at $V_{CE} = 12$ V, $I_C = 1.5$ mA and $S \leq 3$, find R_e , R_1 , R_2 . 7

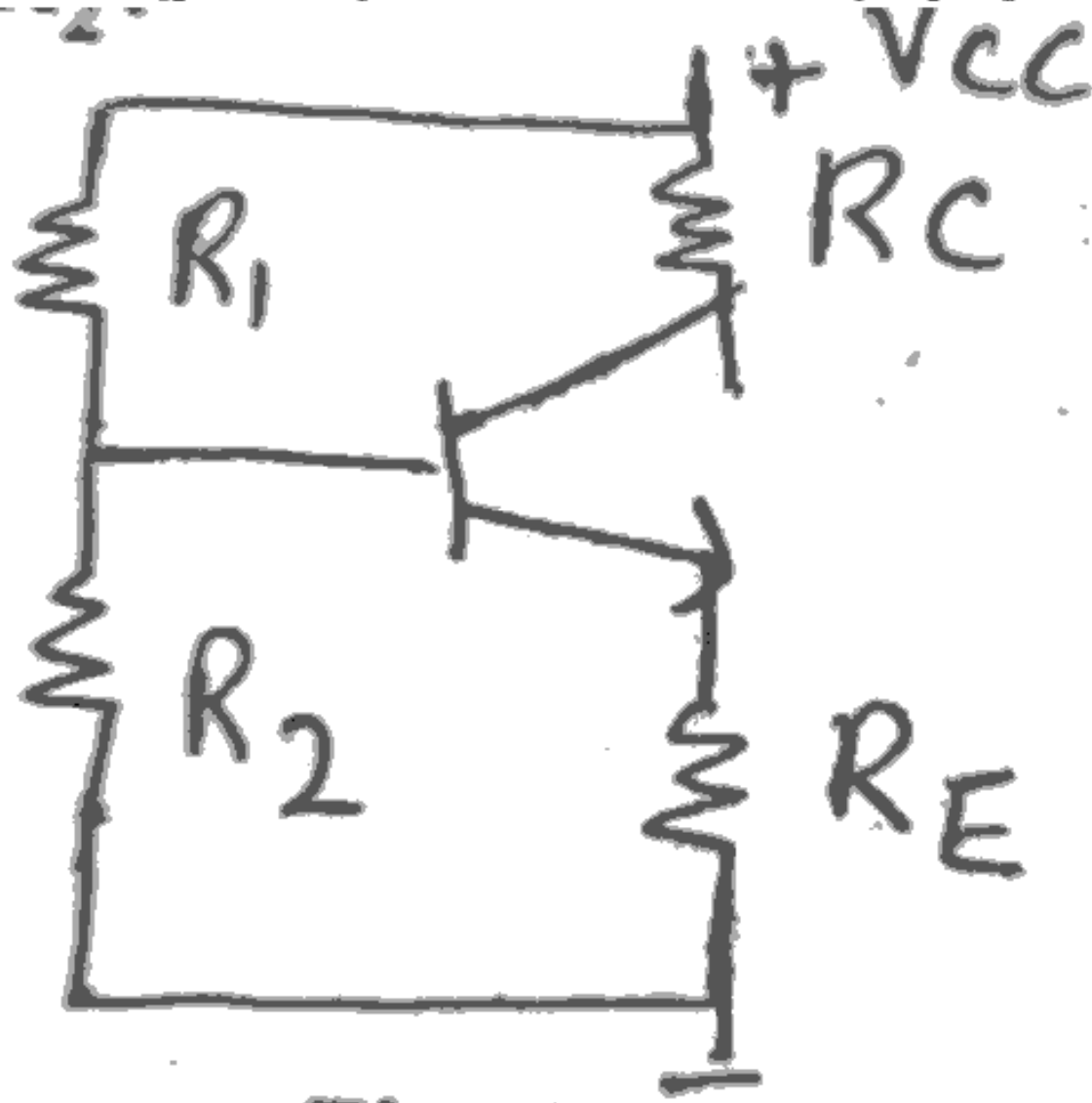

Chapter 5

- 1 Give the comparison of BJT with FET. 2
- 2 Draw and explain drain characteristics and transfer characteristic of JFET. 7
- 3 Explain the working of enhancement MOSFET. 7
- 4 Show that : 7

$$g_m = g_{mo} (1 - V_{gs}/V_p)$$
 and draw small signal FET model.