

**327612(27)**

**BE (6<sup>th</sup> Semester)  
Examination, April-May, 2018  
(Old Scheme)**

**Power Electronic Devices & Applications**

*Time Allowed : 3 hours*                      *Maximum Marks : 80*  
*Minimum Pass Marks : 28*

**Note :** (i) Part (a) of each question is compulsory. Attempt any two from parts (b), (c) and (d) of each question.  
(ii) The figures in the right-hand margin indicate marks.

1. (a) Draw block diagram of a power electronic system. [2]
- (b) Derive the expression of reverse recovery time of diode. The reverse recovery time of a diode is  $t_{rr} = 3 \mu s$  and the rate of fall of the diode current is  $di/dt = 30 A/\mu s$ .  
Determine the storage charge  $Q_{RR}$  and reverse current  $I_{RR}$ . [7]

- (c) Realize diode rectifier circuit with RC load using appropriate expression and waveforms. [7]
- (d) Explain the operation of three-phase bridge rectifier with suitable waveform. [7]
2. (a) Write down the name of component that belongs to thyristor family. [2]
- (b) Draw and explain the  $V-I$  characteristics of thyristor. [7]
- (c) Explain the class-C computation techniques with proper waveform. [7]
- (d) Why does the resistance firing circuit have the limited range of firing angle control between  $0^\circ$  to  $90^\circ$ ? Explain through waveform what will happen if firing angle is increased more than  $90^\circ$ . [7]
3. (a) Draw the Spice model of power BJT. [2]
- (b) Explain the switching characteristics of power BJT. http://www.csvtuonline.com [7]
- (c) Explain IGBT operation and characteristics. [7]
- (d) Give comparison between power BJT and power MOSFET. [7]
4. (a) What do you mean by semiconverter? [2]
- (b) Explain the operation of single-phase full wave converter with its characteristics. [7]

http://www.csvtuonline.com

http://www.csvtuonline.com

http://www.csvtuonline.com

http://www.csvtuonline.com

[ 3 ]

- (c) Explain the AC voltage controller in three-phase half wave controller. [7]
- (d) What are the effects of load inductance on the performance of cyclo-converter? [7]
5. (a) Define AC link chopper. [2]
- (b) Explain the basic principle of a step-up chopper, and derive the equation for minimum and maximum load current for chopper. [7]
- (c) Draw the circuit of class-B chopper circuit and explain its operation with the help of waveforms. [7]
- (d) A single-phase circuit for temperature regulation uses on-off control. The AC input is 230 V, 50 Hz. The circuit has variable frequency TRC. If the i/p goes up by 10%, calculate the percent change required in the triggering of chopper. [7]

<http://www.csvtuonline.com>

Whatsapp @ 9300930012

Your old paper & get 10/-

पुराने पेपर्स भिजे और 10 रुपये पायें,

Paytm or Google Pay से