

328353(28)

BE (3rd Semester)
Examination, Nov.-Dec., 2018
(New Scheme)

Electronic Devices and Circuits

Time Allowed : 3 hours

Maximum Marks : 80


Minimum Pass Marks : 28

- Note :** (i) Attempt all questions. Part (a) of each question is compulsory. Attempt any two parts from (b), (c) and (d) of each question.
(ii) The figures in the right-hand margin indicate marks.

1. (a) State Mass-action Law as an equation and in words. [2]
(b) Explain formation of P-N junction diode and its characteristics. [7]
(c) Prove that for a step-graded p-n junction diode the contact potential is

$$V_0 = V_T \ln \frac{N_D N_A}{n_i^2} \quad [7]$$

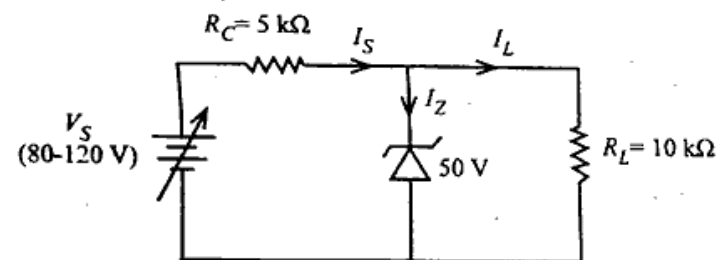- (d) A sample of germanium (Ge) is doped to the extent of 10^{14} donor atoms/cm³ and 7×10^3 acceptor atoms/cm³. At the temperature of the sample the resistivity of intrinsic germanium is 60 Ω-cm. If applied electric field is 2 V/cm, find the total conduction current density. [7]
2. (a) Write the equation of diode current. [2]
(b) Compare half-wave rectifier, full-wave rectifier and bridge rectifier. [7]
(c) Explain Zener diode as voltage regulator. [7]
(d) For the circuit shown, find the maximum and minimum values of Zener diode current. Given that $V_Z = 50$ V, $R_L = 10$ kΩ, $R_S = 5$ kΩ, $V_S = (80$ to 120 V). [7]



3. (a) Define biasing of a transistor. [2]
(b) Draw the input and output characteristics of common emitter configuration. Explain active, saturation and cut-off region. [7]
(c) Explain voltage divider bias circuit and derive the expression for stability factor. [7]


[3]

[4]

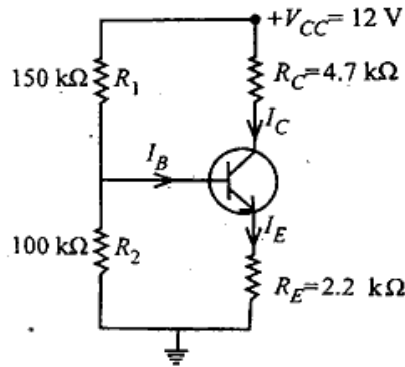- (d) For the circuit shown, find the operating point. What is the stability factor of the circuit?

Given that

$\beta = 50, V_{BE} = 0.7 \text{ V}, V_{CC} = 12 \text{ V}, R_1 = 150 \text{ k}\Omega,$
 $R_C = 4.7 \text{ k}\Omega, R_2 = 100 \text{ k}\Omega, R_E = 2.2 \text{ k}\Omega.$



4. (a) Define pinch-off voltage. [2]
 (b) Explain construction and working of n-channel JFET. <http://www.csvtuonline.com> [7]
 (c) Starting with the definition of g_m and r_d verify the relation $\mu = g_m \times r_d$. Also show that if two identical FET's are connected in parallel. g_m is doubled and r_d is halved. Since $\mu = g_m \times r_d$ then μ remains unchanged. [7]
 (d) Explain FET as voltage variable resistor. [7]

TC-140

(Turn Over)

5. (a) Draw symbol of n-channel E-MOSFET and n-channel D-MOSFET. [2]
 (b) Explain working of Depletion MOSFET with transfer characteristics. [7]
 (c) Explain C-MOS inverter in detail. [7]
 (d) Compare E-MOSFET and D-MOSFET. [7]

»»»»»

TC-140

<http://www.csvtuonline.com>

Whatsapp @ 9300930012
 Your old paper & get 10/-
 पुराने पेपर्स भिजे और 10 रुपये पायें,
 Paytm or Google Pay से