

**325654(25)**

csvtuonline.com

BE (6<sup>th</sup> Semester)

Examination, April-May, 2018

(New Scheme)

**Power Electronics Devices & Circuits**

Time Allowed : 3 hours

Maximum Marks : 80

Minimum Pass Marks : 28

**Note :** (i) Answer all questions. Part (a) of each question is compulsory. Attempt any two parts from (b), (c) and (d) of each question.

(ii) The figures in the right-hand margin indicate marks.


**Unit-I**

csvtuonline.com

1. (a) What is reverse recovery time of SCR ? [2]
- (b) Sketch static I-V characteristic of a thyristor. Label the various voltages, currents and the operating modes and explain. [7]
- (c) Define string efficiency for series/parallel connected SCRs. Derive an expression for the series-connected string. [2+5]

csvtuonline.com (2)

- (d) For the circuit shown in figure below calculate the maximum values of  $\frac{di}{dt}$  and  $\frac{dv}{dt}$  for the thyristor : [7]

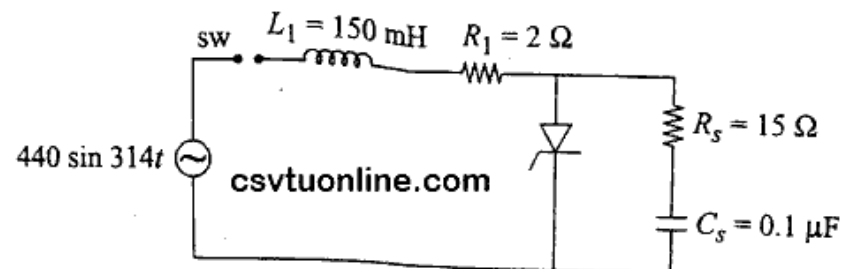**Unit-II**

2. (a) State the difference between half-wave controlled and half-controlled converter. [2]
- (b) What is the effect of source inductance on the operation of single-phase full-bridge converter ? Derive the expression for output voltage, including the effect of source inductance. [2+5]
- (c) A single-phase full-bridge converter operating from a 230 V, 50 Hz supply feeds a load comprising a d.c. source of voltage 220 V, resistance of 3 Ω and an infinite inductance. The a.c. source inductance is 1 mH. Converter operates in the inverting mode with a firing delay angle  $\alpha = 120^\circ$ . Calculate the average value of load current, overlap angle and margin angle. [7]

TC-260

csvtuonline.com

(Continued)

(3)

csvtuonline.com

- (d) Explain how two  $1-\phi$  full converters can be connected back-to-back to form a circulating current type of dual converter. [7]

### Unit-III

3. (a) Write any two applications of chopper. [2]
- (b) Discuss the technique of obtaining variable d.c. voltage. Hence, derive the expression for step-up chopper using SCR. [4+3]
- (c) A d.c. step-down chopper has a resistive load  $R = 10 \Omega$  and input voltage  $V_s = 200 \text{ V}$ . When the chopper remains on, its voltage drop is  $2 \text{ V}$ . The chopper frequency is  $1 \text{ kHz}$ . If duty cycle is  $50\%$ , determine—
- (i) average output voltage ;
  - (ii) r.m.s. output voltage ;
  - (iii) chopper efficiency ;
  - (iv) effective input resistance of chopper. [7]
- (d) Explain the voltage-commutated chopper along with various waveforms. Also write the merits and demerits of voltage-commutated chopper. [5+2]

### Unit-IV

csvtuonline.com

4. (a) What is an inverter? [2]
- (b) Compare the voltage source inverters with current source inverters. [7]

csvtuonline.com (4)

- (c) Explain the operation of  $180^\circ$  mode 3-phase bridge inverter feeding a delta-connected resistive load. [7]
- (d) Design a series inverter circuit for operation in the frequency range  $1 \text{ kHz}$  to  $5 \text{ kHz}$ . The load resistance may vary from  $25 \Omega$  to  $100 \Omega$ . The peak load current is limited to  $3 \text{ A}$  and the supply voltage is  $100 \text{ V}$ . [7]

### Unit-V

5. (a) Write any two applications of cycloconverter. [2]
- (b) Describe the basic working principle of a single-phase to single-phase bridge type cycloconverter. Sketch the output voltage and current waveforms for a resistive load. [7]
- (c) A single-phase unidirectional voltage controller is connected to a load of  $R = 10 \Omega$ . Input voltage is  $230 \text{ V}$ ,  $50 \text{ Hz}$ . Firing delay is  $30^\circ$ . Determine (i) r.m.s. value of output voltage, (ii) average and r.m.s. values of thyristor current and (iii) input power factor. [7]
- (d) Describe the principle of phase control in single-phase half-wave voltage controller. Derive the expressions for the average and r.m.s. value of output voltage for this voltage controller. [4+3]