

328453(28)

B. E. (Fourth Semester) Examination,
April-May 2016

(New Scheme)

(ET & T Engg.)

ANALOG ELECTRONICS

Time Allowed : Three hours

Maximum Marks : 80

Minimum Pass Marks : 28

Note : In each question part (a) is compulsory and carry 2 marks. Solve any two parts from (b), (c) & (d) and carry 7 marks.

Unit I

(a) What are the limitations of h-parameter model? 2

(b) Express common base h parameters in terms of common collector h parameters. 7

328453(28)

(c) Derive the expression for R_i , A_v and R_o in Darlington pair. 7

(d) For the circuit shown in fig. 1 find the voltage gain

$\left(\frac{V_o}{V_s} \right)$ and input impedance as a function of R_s, b, R_e

and R_L . Assume that $h_{oe}(R_e + R_L) \ll 0.1$.

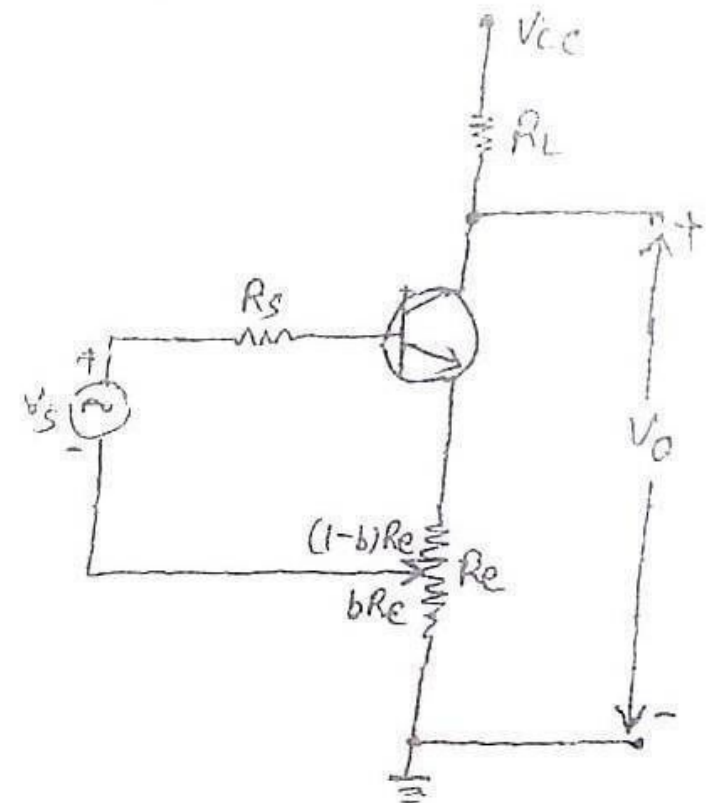


Fig. 1

328453(28)

www.csvtuonline.com

www.csvtuonline.com

Unit-II

2. (a) What is the criteria for validity of h-pi parameter? 2
- (b) Derive the expression for f_H for emitter follower at high frequency. 7
- (c) Derive the expression for $|A_{v50}, f_H|$ for CE amplifier. 7
- (d) Given the following transistor measurements made at $i_c = 5 \text{ mA}$, $V_{CE} = 10 \text{ V}$ and room temperature :
- $h_{fe} = 100$, $h_{ie} = 600 \Omega$, $|A_{ie}| = 10$ at MHz, $C_c = 3 \text{ pF}$. Find f_β , f_T , C_e , $r_{b'e}$ and r_{bb} . 7

Unit-III

3. (a) What is distortion in amplifier? 2
- (b) Explain the step response of an amplifier at low frequency and high frequency. 7
- (c) Prove that the bandwidth shrinks in cascading of identical non-interacting stages. 7
- (d) Explain different types of coupling amplifiers. 7