

CSVТУonline.com

Chapter 1

- 1 What is Gray code ? Convert Gray code 100011101 to binary ? **2**
- 2 Simplify the following function by using Quine-McCluskey method **7**
:
 $f(A,B,C,D) = \sum m(1,4,6,7,8,9,10,11,15)$.
- 3 Minimize the following expression using K-map and realize using **7**
logic gates :
 $F1(A,B,C,D) = \sum m(1,3,5,8,9,11,15) + d(2,13)$
 $F2(A,B,C,D) = \pi M(1,2,3,5,6,7,9,10,11,13,14,15)$
- 4 Simplify the following Boolean identity : **7**
(i) $(\{ AB + \bar{A}\bar{C} + A\bar{B}C(A\bar{B} + C) \})$

Chapter 2

- 1 What is meant by Fan-in and Fan-out ? **2**
- 2 Explain the working of CMOS inverter giving its circuit diagram **7**
and explain CMOS-NOR gate function.
- 3 Draw the circuit of tri-state TTL gate and explain it. **7**
- 4 What are the characteristics of the ECL family ? With the help of **7**
a neat circuit diagram, explain the working of a two input ECL
OR/NOR gate.

Chapter 3

CSVТУonline.com

- 1 What is the difference between multiplexer and decoder. **2**
- 2 Design BCD to Excess 3 code converter using AND, OR, EX-OR. **7**

- 3 Design 16 : 1 multiplexer using 4 : 1 multiplexer. 7
- 4 Explain the operation of four bit carry-look ahead adder circuit. 7

Chapter 4

- 1 Compare between Synchronous and Asynchronous sequential circuit ? 2
- 2 What is shift register ? With neat diagram explain working of Parallel-in, Serial-out shift register. 7
- 3 Implement logic to convert S-R flip flop to T flip flop. 7
- 4 Design mod-10 counter using jk flip flop. 7

Chapter 5

- 1 Explain the difference between static and dynamic memory ? 2
 - 2 Implement the following Boolean function using PLA : 7
 $f_1(A,B,C) = \Sigma(0,1,3,4)$
 $f_2(A,B,C) = \Sigma(1,2,3,4,5)$
- CSVТУonline.com**
- 3 What is a programmable logic array ? Also explain its advantage and disadvantage. 7
 - 4 Explain briefly the different type of ROMs. 7